

modulation levels due to AC shunting of the audio signal).

The modified and the original circuits are shown below, with the modified AGC line highlighted in blue.

Notes

1. R5 (cathode bias resistor for 6C6) should not be allowed to drift much above its value of $15k\Omega$ because the valve is already operating near its cutoff point.

